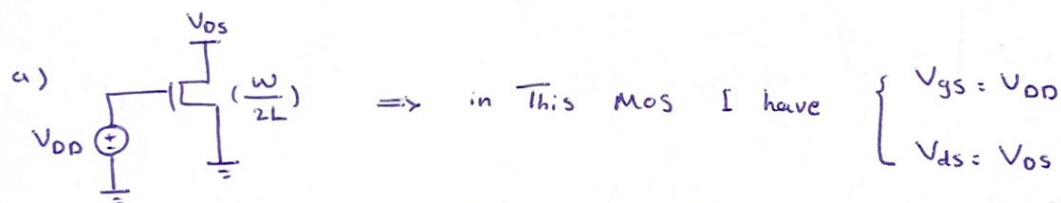



2.2:

Reza Adinepour
402131055

$$I_{DS} : \begin{cases} 0 & ; V_{gs} < V_{th} \quad (\text{cutoff}) \\ \beta (V_{gs} - V_{th} - \frac{V_{ds}}{2}) V_{ds} & ; V_{ds} < V_{ds,sat} \quad (\text{Linear}) \\ \frac{\beta}{2} (V_{gs} - V_{th})^2 & ; V_{ds} > V_{ds,sat} \quad (\text{Saturation}) \end{cases}$$


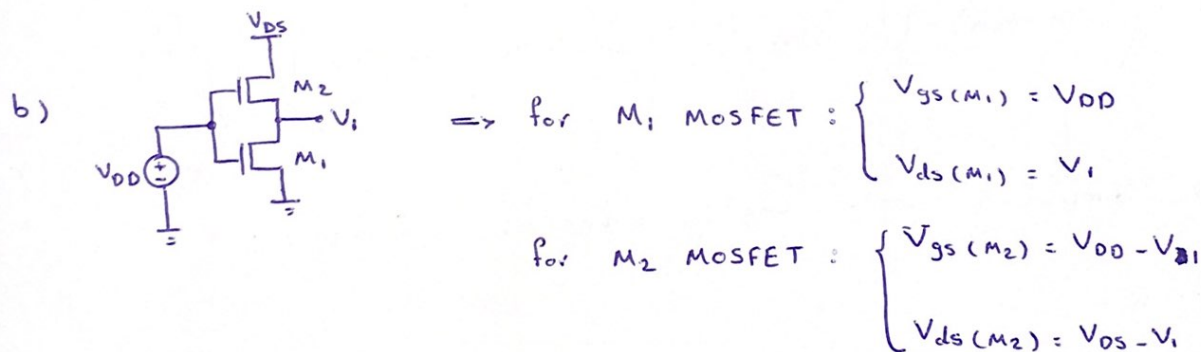
$$\text{So, } I_{DS(a)} = K \frac{W}{2L} \left(V_{DD} - V_{th} - \frac{V_{DS}}{2} \right) V_{DS}$$



So, [know $I_{DS}(M_1) = I_{DS}(M_2)$:

$$\frac{K_1 W}{L} \left[V_{DD} - V_{th} - \frac{V_i}{2} \right] V_i = \frac{K_2 W}{L} \left[(V_{DD} - V_i) - V_{th} - \frac{1}{2} (V_{DS} - V_i) \right] (V_{DS} - V_i)$$

$$\Rightarrow V_i = (V_{DD} - V_{th}) - \left[(V_{DD} - V_{th})^2 - \left(V_{DD} - \frac{1}{2} V_{DS} - V_{th} \right) V_{DS} \right]^{\frac{1}{2}} \quad (I)$$

Thus : $I_{DS}(M_1) = K \frac{W}{L} \left(V_{DD} - V_{th} - \frac{V_i}{2} \right) V_i \xrightarrow{(I)}$

$$I_{DS}(M_1) = K \frac{W}{L} \left[V_{DD} - V_{th} - \frac{1}{2} \left((V_{DD} - V_{th}) - \left(V_{DD} - \frac{1}{2} V_{DS} - V_{th} \right) V_{DS} \right)^{\frac{1}{2}} \right] \times V_i$$

$$\Rightarrow I_{DS(M_1)} = K \frac{W}{L} \left[V_{DD} - V_{th} \dots \right.$$

$$\left. - \frac{1}{2} \left((V_{DD} - V_{th}) - \left(V_{DD} - \frac{1}{2} V_{DS} - V_{th} \right) V_{DS} \right)^{\frac{1}{2}} \times \left((V_{DD} - V_{th}) - \left[(V_{DD} - V_{th})^2 - \left(V_{DD} - \frac{1}{2} V_{DS} - V_{th} \right) V_{DS} \right]^{\frac{1}{2}} \right) \right]$$


$$\Rightarrow I_{DS(M_2)} = K \frac{W}{L} \left[V_{DD} - \left((V_{DD} - V_{th}) - \left((V_{DD} - V_{th})^2 - \left(V_{DD} - \frac{1}{2} V_{DS} - V_{th} \right) V_{DS} \right)^{\frac{1}{2}} \right) \right]$$

$$- V_{th} - \frac{1}{2} \left(V_{DS} - \left((V_{DD} - V_{th}) - \left((V_{DD} - V_{th})^2 - \left(V_{DD} - \frac{1}{2} V_{DS} - V_{th} \right) V_{DS} \right)^{\frac{1}{2}} \right) \right)$$

$$\times \left(V_{DS} - \left((V_{DD} - V_{th}) - \left((V_{DD} - V_{th})^2 - \left(V_{DD} - \frac{1}{2} V_{DS} - V_{th} \right) V_{DS} \right)^{\frac{1}{2}} \right) \right)$$

after simplifying $\Rightarrow I_{DS(M_1)} = I_{DS(M_2)} = 2 I_{DS(a)}$

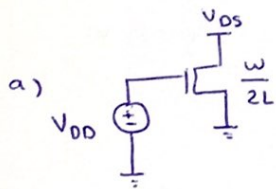2.3 : consider body effect and calculate $I_{DS1} = I_{DS2}$ or $I_{DS1} > I_{DS2}$ or $I_{DS1} < I_{DS2}$



in this section I know :

$$\begin{cases} V_{GS} = V_{DD} \\ V_{DS} = V_{DS} \\ V_{SB} = V_S - V_B = -V_B \end{cases}$$


→ if body and source are short circuit from the inside of transistor, we have : $V_{SB} = 0$

** Assumption ** in this question we assume that the source and the body of the transistor are short circuit.

$$\text{So: } V_t = V_{t0} + \gamma \left(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s} \right) \xrightarrow{V_{sb}(M_1)=0} V_t = V_{t0} + \gamma \left(\sqrt{\phi_s + 0} - \sqrt{\phi_s} \right)$$

$\Rightarrow V_t = V_{t0} = V_{th} \rightarrow$ no changed threshold voltage for M_1 transistor
so the current no changing.

but for section b :

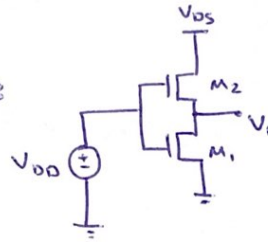

$$M_1 \begin{cases} V_{gs} = V_{DD} \\ V_{ds} = V_i \\ V_{sb} = V_s - V_b = 0 \rightarrow \text{no changed } I_s \end{cases}$$

$$M_2 \begin{cases} V_{gs} = V_{DD} - V_{os} \\ V_{ds} = V_i - V_{os} \\ V_{sb} = V_{os} - V_b > 0 \end{cases}$$

in M_2 transistor V_{sb} voltage is changed and the current changed as follows :

$$I_{DS2} = \frac{k\omega}{L} \left[(V_{DD} - V_{os}) - V_{t0} - \gamma \left(\sqrt{\phi_s + V_{os} - V_b} - \sqrt{\phi_s} \right) - \frac{1}{2} (V_i - V_{os}) \right] (V_i - V_{os})$$

from the previous part I know : $I_{DS1} = k \frac{\omega}{2L} \left(V_{DD} - V_{th} - \frac{V_{os}}{2} \right) V_{os}$

\Rightarrow So, considering the body effect, the threshold voltage has increase for M_2 transistor and the I_{DS} decreases $\Rightarrow I_{DS2} < I_{DS1}$

2.6 : prove this equation : ~~XXXXXXXXXX~~ $V_{dsat} = \frac{\bar{V}_{GT} \bar{V}_c}{\bar{V}_{GT} + \bar{V}_c}$

$$I \text{ know : } I_{ds} = \begin{cases} \frac{\mu_{eff}}{1 + \frac{V_{ds}}{V_c}} C_{ox} \frac{\omega}{L} \left(V_{GT} - \frac{V_{ds}}{2} \right) V_{ds} & ; V_{ds} < V_{d,sat} \quad (\text{Linear}) \\ C_{ox} \omega (V_{GT} - V_{d,sat}) V_{sat} & ; V_{ds} > V_{d,sat} \quad (\text{Saturation}) \end{cases}$$

in $V_{ds} = V_{ds,sat}$ two part of equation is equal. So I replace V_{ds} with $V_{ds,sat}$ in both and I make them equal :

$$I_{ds} = \begin{cases} \frac{\mu_{eff}}{1 + \frac{V_{ds,sat}}{V_c}} C_{ox} \frac{W}{L} \left(V_{GT} - \frac{V_{ds,sat}}{2} \right) V_{ds,sat} \\ C_{ox} W (V_{GT} - V_{d,sat}) V_{sat} \end{cases}$$

$$\Rightarrow \cancel{C_{ox} W} (V_{GT} - V_{d,sat}) V_{sat} = \frac{\mu_{eff}}{1 + \frac{V_{ds,sat}}{V_c}} \cancel{C_{ox} \frac{W}{L}} \left(V_{GT} - \frac{V_{d,sat}}{2} \right) V_{d,sat}$$

$$\Rightarrow (V_{GT} - V_{d,sat}) V_{sat} = \frac{\mu_{eff}}{L \left(1 + \frac{V_{d,sat}}{V_c} \right)} \left(V_{GT} - \frac{V_{d,sat}}{2} \right) V_{d,sat}$$

$$\Rightarrow -V_{sat} V_{d,sat} = -V_{sat} V_{GT} + \frac{\mu_{eff}}{L \left(1 + \frac{V_{d,sat}}{V_c} \right)} \left(V_{GT} - \frac{V_{d,sat}}{2} \right) V_{d,sat}$$

$$\Rightarrow (V_{GT} - V_{d,sat}) V_{sat} = V_{GT} V_{d,sat} \times \frac{V_c \mu_{eff}}{L (V_c + V_{d,sat})} - \frac{V_{d,sat}^2}{2} \times \frac{V_c \mu_{eff}}{L (V_c + V_{d,sat})}$$

after solve this second order equation we can find: $V_{d,sat} = \frac{V_{GT} V_c}{V_{GT} + V_c}$

2.7 : $\begin{cases} \text{Process} = 0.6 \mu\text{m} \\ \text{gate oxide thickness} = 100 \text{ \AA} = 100 \times 10^{-8} \text{ m} \\ N_A = 2 \times 10^{17} \text{ cm}^{-3} \\ V_{th0} = 0.7 \text{ V}, V_{sb} = 4 \text{ V} \rightarrow \text{if } V_{sb} = 0 \rightarrow V_{th} = 0.7 \text{ No changed} \end{cases}$

in first I should calculate surface potential at threshold:

$$\phi_s = 2 V_{thermal} \ln \left(\frac{N_A}{n_i} \right) \xrightarrow[V_{thermal} = 0.026 \text{ V}]{n_i = 1.45 \times 10^{10}} \phi_s = 2 \times 0.026 \times \ln \left(\frac{2 \times 10^{17}}{1.45 \times 10^{10}} \right) = \underline{0.854 \text{ V}}$$

in this part I want calculate body effect coefficient:

$$\gamma = \frac{t_{ox}}{C_{ox}} \sqrt{2q \epsilon_{si} N_A} = \frac{\sqrt{2q \epsilon_{si} N_A}}{C_{ox}} = \frac{100 \times 10^{-8}}{3.9 \times 8.85 \times 10^{-14}} \times \sqrt{2 \times 1.6 \times 10^{-19} \times 11.7 \times 8.85 \times 10^{-14} \times 2 \times 10^{17}} \\ = 0.745$$

$$\Rightarrow V_{th} = V_{th0} + \gamma \left(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s} \right) = 0.7 + 0.745 \left(\sqrt{0.854 + 4} - \sqrt{0.854} \right) = \underline{1.65 \text{ V}}$$

2.8 : No, any number of transistors may be ~~rep~~ placed in series
 Although the delay increases with the square of the number of series transistor.

2.9 : The threshold is increased by applying a negative body voltage
 So $\bar{V}_{sb} > 0$

2.10 :
$$\begin{cases} V_{th} = 0.4 \text{ V} \\ V_{DD} = 1.2 \text{ V} \end{cases}$$

a)
$$\frac{(V_{DD} - 0.3)^2}{(V_{DD} - 0.4)^2} = \frac{(1.2 - 0.3)^2}{(1.2 - 0.4)^2} = 1.26$$

b)
$$e^{\frac{-V_{th}}{nV_{thermal}}} = \frac{e^{\frac{-0.3}{1.4 \times 0.026}}}{e^{\frac{-0.4}{1.4 \times 0.026}}} = 15.6$$

c)
$$V_{thermal} = \frac{k_B T}{q} = \frac{1.38 \times 10^{-23} \times 393}{1.6 \times 10^{-19}} = \boxed{34 \text{ mV}} \Rightarrow \frac{e^{\frac{-0.3}{1.4 \times 0.034}}}{e^{\frac{-0.4}{1.4 \times 0.034}}} = 8.2$$

$120^\circ \text{C} \rightarrow 393 \text{ K}$

$$k_B = 1.381 \times 10^{-23} \frac{\text{J}}{\text{K}} = 8.617 \times 10^{-5} \frac{\text{eV}}{\text{K}}$$

* The total leakage will normally be higher for both threshold voltages at high temperature