
 


2.16 :

 

I should equalize the current of the transistors in the B region.

In B region

$$\begin{cases} \text{nMOS in saturation} & \Rightarrow \frac{K'_n}{2} (V_{gs} - V_{th,n})^2 = I_{ds(n)} \\ \text{pMOS in linear} & \Rightarrow \frac{K'_p}{2} \left[V_{gs} - V_{th,p} - \frac{V_{ds}}{2} \right] V_{ds} = I_{ds(p)} \end{cases}$$

$$\Rightarrow I_{ds(n)} = I_{ds(p)} \quad \Rightarrow (V_{gs} - V_{th,n})^2 = (V_{gs} - V_{th,p} - \frac{V_{ds}}{2}) V_{ds} \quad \xrightarrow{V_{th,n} = V_{th,p} = V_{th}}$$

$$\Rightarrow (V_{in} - V_{th})^2 = (V_{in} - V_{out} + V_{th} - \frac{1}{2}(V_{out} - V_{DD})) (V_{out} - V_{DD})$$

$$\Rightarrow V_{in}^2 + V_{th}^2 - 2V_{in}V_{th} = V_{out}V_{in} - V_{out}^2 + V_{out}V_{th} - \frac{1}{2}V_{out}^2 + \frac{1}{2}V_{out}V_{DD} - V_{in}V_{DD} + V_{out}V_{DD} - V_{th}V_{DD} + \frac{1}{2}V_{out}V_{DD} - \frac{1}{2}V_{DD}^2$$

$$\Rightarrow V_{in}^2 + V_{th}^2 + V_{in}V_{DD} - 2V_{in}V_{th} + V_{DD}V_{th} + \frac{1}{2}V_{DD}^2 = V_{out} \left[V_{in} - V_{out} + V_{th} - \frac{1}{2}V_{out} + \frac{1}{2}V_{DD} + V_{DD} + \frac{1}{2}V_{DD} \right]$$

$$\Rightarrow V_{out} = (V_{in} + V_{th}) + \left[(V_{in} + V_{th})^2 - (V_{in} - V_{th})^2 + V_{DD}(V_{DD} - 2V_{in} - 2V_{th}) \right]^{\frac{1}{2}}$$

Repeat this calculation for D region \rightarrow

$$\begin{cases} \text{PMOS in saturation} \\ \text{nMOS in Linear} \end{cases}$$

$$\Rightarrow K'_n \frac{\omega}{L} \left[V_{gs} - V_{th,n} - \frac{V_{ds}}{2} \right] V_{ds} = K'_p \frac{\omega}{L} (V_{gs} - V_{th,p})^2 \xrightarrow{V_{th,p} = V_{th,n}}$$

$$\Rightarrow \left(V_{in} - V_{th} - \frac{1}{2} V_{out} \right) V_{out} = (V_{in} - V_{DD} + V_{th})^2 \Rightarrow V_{out} = (V_{in} - V_{th}) - \sqrt{(V_{in} - V_{th})^2 - (V_{DD} - V_{in} - V_{th})^2}$$

2.17: noise margin for Inverter operating at 1^V with $V_{tn} = |V_{tp}| = 0.35^V$, $\beta_p = \beta_n$

we must calculate $\frac{dV_{out}}{dV_{in}}$ at D and B point.

I) for point B: $V_{out} = (V_{in} + V_t) + \left[(V_{in} + V_t)^2 - (V_{in} - V_t)^2 + V_{DD} (V_{DD} - 2V_{in} - 2V_t) \right]^{\frac{1}{2}}$

$$\xrightarrow[V_t = 0.35^V]{V_{DD} = 1^V} V_{out} = (V_{in} + 0.35) + \sqrt{(V_{in} + 0.35)^2 - (V_{in} - 0.35)^2 + 1(1 - 2V_{in} - 2(0.35))}$$

$$\begin{cases} V_{in} \geq 1.89^V \rightarrow V_{out} \text{ is complex} \rightarrow \text{unacceptable} \\ V_{in} \leq 0.408^V \rightarrow V_{out} = 0.781^V \checkmark \end{cases} \rightarrow \begin{cases} V_{IL} = 0.408^V \\ V_{OH} = 0.781^V \end{cases}$$

II) for point D: $V_{out} = (V_{in} - V_t) - \sqrt{(V_{in} - V_t)^2 - (V_{DD} - V_{in} - V_t)^2} \xrightarrow[V_t = 0.35]{V_{DD} = 1}$


$$V_{out} = (V_{in} - 0.35) - \sqrt{(V_{in} - 0.35)^2 - (1 - V_{in} - 0.35)^2}$$

$$\Rightarrow \begin{cases} V_{in} \geq 0.5^V \rightarrow V_{out} = 0.15^V \\ V_{in} \leq 0.408^V \rightarrow V_{out} = 0.781^V \end{cases} \Rightarrow \begin{cases} V_{IH} = 0.5^V \\ V_{OL} = 0.15^V \end{cases}$$


$$NM_H = V_{OH} - V_{IH} = 0.781 - 0.5 = \boxed{0.281^V}$$

$$NM_L = V_{IL} - V_{OL} = 0.408 - 0.15 = \boxed{0.258^V}$$


2.20 :

 

 
Pass transistor Pass 0
because nMOS transistor Pass
strong 0



Pass transistor Pass $|V_{tp}|$
because pMOS transistor Pass
strong 1 and degraded 0

 

PMOS transistor pass $|V_{tp}|$
and nMOS Transistor pass the same
 $|V_{tp}|$

 

PMOS transistor pass 1 and nMOS
transistor pass $V_{DD} - V_{tn}$ because
degraded 1